

Improving SDR based on QSD at low frequencies (typically 50 – 500 Khz)

SDR (Software Defined Radio) receivers widely use direct I&Q direct baseband conversion .

The typical circuits used are QSD (Quadrature Sampling Detectors) .

This circuits allows high IP3 values but they are built with switches driven from square waves .

This means that the conversion process works not only at the fundamental frequency but also at all the harmonics .

The square waves have very rich harmonic odd content .

For example the third harmonic is only 17 dB below the fundamental .

This means that a receiver based on QSD receive at the third harmonic of the OL with only 17 dB of attenuation !

At frequencies from around 1.5 to 30 Mhz , to avoid this problem , it could be easy to design a good internal preselector with double tuned tracking bandpass filter , and this was done in designing Ciao Radio H101: <http://www.comsistel.com/Ciao%20Radio.htm> .

Under this frequencies , the coils and capacitors become quite large (in value and dimensions) , lossy , and expensive .

Fr this reason there is only one lowpass filter at 1.6 Mhz , for receiving the frequencies under this limit that allow very sharp receptions till around 560 Khz .

To avoid the problem of odd harmonics at lower frequencies , the best way is to use a bank of low pass filters .

Some examples :

Band definitions :

LF Broadcasting Band : 153-279 Khz .

NDB (Non Directional Beacons) : 190-535 Khz

MF Broadcasting Band : 535-1705 Khz

1) If you want to receive 75 Khz or 77.5 Khz , time and frequency stations , the third harmonic lie at 225 and 232.5 Khz , where very strong LF broadcasting signals are present .

2) If you want to receive in the LF band , at 270 Khz , the third harmonic lies at 810 Khz , where very strong MF broadcasting signals are present .

3) If you want to receive at 535 Khz , the third harmonic lies at 1605 Khz , where other very strong broadcasting signals are present .

A possible solution :

For several other uses , I have a blackbox on the table of the lab where some lowpass filters are switched between two BNC connectors .

This could be a solution and the drawing is attached .

I have used the common values I had in the shack approaching the values calculated from the Software RFSIMM99 .

For improving the performance of Ciao Radio H101 between 50 and 600 Khz , of course only the first four low pass are eventually needed if not using at this frequencies antennas with passband behaviours .

A special filter tailored for the NDB band as been designed on the side .

Claudio Re IIRFQ - 07 April 2007

